

Michael Faraday 1791-1867

# Physics 2113


## Lecture 30: FRI 7 NOV

### CH30: Induction and Inductance



Problems

•4 A wire loop of radius 12 cm and resistance  $8.5\ \Omega$  is located in a uniform magnetic field  $\vec{B}$  that changes in magnitude as given in Fig. 30-33. The vertical axis scale is set by  $B_s = 0.50\ \text{T}$ , and the horizontal axis scale is set by  $t_s = 6.00\ \text{s}$ . The loop's plane is perpendicular to  $\vec{B}$ . What emf is induced in the loop during time intervals (a) 0 to 2.0 s, (b) 2.0 s to 4.0 s, and (c) 4.0 s to 6.0 s?

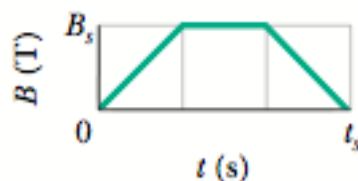

**Fig. 30-33** Problem 4.

4. (a) We use  $\varepsilon = -d\Phi_B/dt = -\pi r^2 dB/dt$ . For  $0 < t < 2.0\ \text{s}$ :


$$\varepsilon = -\pi r^2 \frac{dB}{dt} = -\pi (0.12\text{m})^2 \left( \frac{0.5\text{T}}{2.0\text{s}} \right) = -1.1 \times 10^{-2}\ \text{V}.$$

(b) For  $2.0\ \text{s} < t < 4.0\ \text{s}$ :  $\varepsilon \propto dB/dt = 0$ .

(c) For  $4.0\ \text{s} < t < 6.0\ \text{s}$ :

$$\varepsilon = -\pi r^2 \frac{dB}{dt} = -\pi (0.12\text{m})^2 \left( \frac{-0.5\text{T}}{6.0\text{s} - 4.0\text{s}} \right) = 1.1 \times 10^{-2}\ \text{V}.$$

•3 **SSM WWW** In Fig. 30-32, a 120-turn coil of radius 1.8 cm and resistance  $5.3 \, \Omega$  is coaxial with a solenoid of 220 turns/cm and diameter 3.2 cm. The solenoid current drops from 1.5 A to zero in time interval  $\Delta t = 25$  ms. What current is induced in the coil during  $\Delta t$ ?

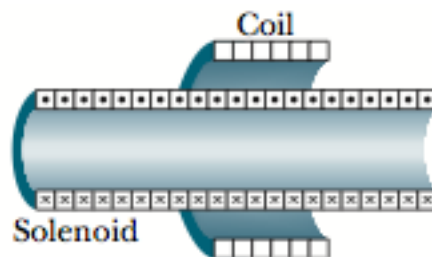

**Fig. 30-32** Problem 3.

3. **THINK** Changing the current in the solenoid changes the flux, and therefore, induces a current in the coil.

**EXPRESS** Using Faraday's law, the total induced emf is given by

$$\mathcal{E} = -N \frac{d\Phi_B}{dt} = -NA \left( \frac{dB}{dt} \right) = -NA \frac{d(\mu_0 ni)}{dt} = -N\mu_0 nA \frac{di}{dt} = -N\mu_0 n(\pi r^2) \frac{di}{dt}$$

By Ohm's law, the induced current in the coil is  $i_{\text{ind}} = |\mathcal{E}| / R$ , where  $R$  is the resistance of the coil.

**ANALYZE** Substituting the values given, we obtain

$$\begin{aligned} \mathcal{E} &= -N\mu_0 n(\pi r^2) \frac{di}{dt} = -(120)(4\pi \times 10^{-7} \text{ T} \cdot \text{m/A})(22000/\text{m})\pi(0.016 \text{ m})^2 \left( \frac{1.5 \text{ A}}{0.025 \text{ s}} \right) \\ &= 0.16 \text{ V}. \end{aligned}$$

$$\text{Ohm's law then yields } i_{\text{ind}} = \frac{|\mathcal{E}|}{R} = \frac{0.16 \text{ V}}{5.3 \, \Omega} = 0.030 \text{ A}.$$


**LEARN** The direction of the induced current can be deduced from Lenz's law, which states that the direction of the induced current is such that the magnetic field which it produces opposes the change in flux that induces the current.


•44 A 12 H inductor carries a current of 2.0 A. At what rate must the current be changed to produce a 60 V emf in the inductor?

44. Since  $\varepsilon = -L(di/dt)$ , we may obtain the desired induced emf by setting

$$\frac{di}{dt} = -\frac{\varepsilon}{L} = -\frac{60\text{V}}{12\text{H}} = -5.0\text{A/s},$$

or  $|di/dt| = 5.0\text{A/s}$ . We might, for example, uniformly reduce the current from 2.0 A to zero in 40 ms.

**•57**  In Fig. 30-63,  $R = 15\ \Omega$ ,  $L = 5.0\ \text{H}$ , the ideal battery has  $\mathcal{E} = 10\ \text{V}$ , and the fuse in the upper branch is an ideal  $3.0\ \text{A}$  fuse. It has zero resistance as long as the current through it remains less than  $3.0\ \text{A}$ . If the current reaches  $3.0\ \text{A}$ , the fuse “blows” and thereafter has infinite resistance. Switch  $S$  is closed at time  $t = 0$ . (a) When does the fuse blow? (*Hint:* Equation 30-41 does not apply. Rethink Eq. 30-39.) (b) Sketch a graph of the current  $i$  through the inductor as a function of time. Mark the time at which the fuse blows.

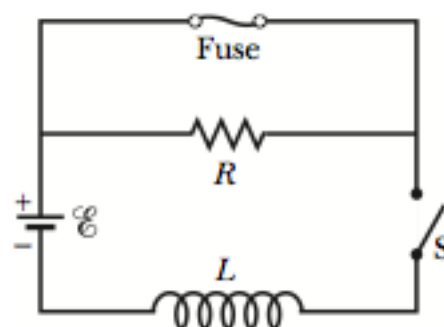

**Fig. 30-63** Problem 57.

57. (a) Before the fuse blows, the current through the resistor remains zero. We apply the loop theorem to the battery-fuse-inductor loop:  $\mathcal{E} - L \, di/dt = 0$ . So  $i = \mathcal{E}t/L$ . As the fuse blows at  $t = t_0$ ,  $i = i_0 = 3.0\ \text{A}$ . Thus,

$$t_0 = \frac{i_0 L}{\mathcal{E}} = \frac{(3.0\ \text{A})(5.0\ \text{H})}{10\ \text{V}} = 1.5\ \text{s}.$$

**•63 ILW** At  $t = 0$ , a battery is connected to a series arrangement of a resistor and an inductor. If the inductive time constant is 37.0 ms, at what time is the rate at which energy is dissipated in the resistor equal to the rate at which energy is stored in the inductor's magnetic field?

63. From Eq. 30-49 and Eq. 30-41, the rate at which the energy is being stored in the inductor is

$$\frac{dU_B}{dt} = \frac{d(Li^2/2)}{dt} = Li \frac{di}{dt} = L \left( \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L}) \right) \left( \frac{\mathcal{E}}{R} \frac{1}{\tau_L} e^{-t/\tau_L} \right) = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L}) e^{-t/\tau_L}$$

where  $\tau_L = L/R$  has been used. From Eq. 26-22 and Eq. 30-41, the rate at which the resistor is generating thermal energy is

$$P_{\text{thermal}} = i^2 R = \frac{\mathcal{E}^2}{R^2} (1 - e^{-t/\tau_L})^2 R = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L})^2.$$

We equate this to  $dU_B/dt$ , and solve for the time:

$$\frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L})^2 = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L}) e^{-t/\tau_L} \Rightarrow t = \tau_L \ln 2 = (37.0 \text{ ms}) \ln 2 = 25.6 \text{ ms}.$$

•68 A toroidal inductor with an inductance of 90.0 mH encloses a volume of  $0.0200 \text{ m}^3$ . If the average energy density in the toroid is  $70.0 \text{ J/m}^3$ , what is the current through the inductor?

68. The magnetic energy stored in the toroid is given by  $U_B = \frac{1}{2} Li^2$ , where  $L$  is its inductance and  $i$  is the current. By Eq. 30-54, the energy is also given by  $U_B = u_B \mathcal{V}$ , where  $u_B$  is the average energy density and  $\mathcal{V}$  is the volume. Thus

$$i = \sqrt{\frac{2u_B \mathcal{V}}{L}} = \sqrt{\frac{2(70.0 \text{ J/m}^3)(0.0200 \text{ m}^3)}{90.0 \times 10^{-3} \text{ H}}} = 5.58 \text{ A} .$$

**47** *Inductors in series.* Two inductors  $L_1$  and  $L_2$  are connected in series and are separated by a large distance so that the magnetic field of one cannot affect the other. (a) Show that the equivalent inductance is given by

$$L_{\text{eq}} = L_1 + L_2.$$

47. (a) Voltage is proportional to inductance (by Eq. 30-35) just as, for resistors, it is proportional to resistance. Since the (independent) voltages for series elements add ( $V_1 + V_2$ ), then inductances in series must add,  $L_{\text{eq}} = L_1 + L_2$ , just as was the case for resistances. Note that to ensure the independence of the voltage values, it is important that the inductors not be too close together (the related topic of mutual inductance is treated in Section 30-12). The requirement is that magnetic field lines from one inductor should not have significant presence in any other.

(b) Just as with resistors,  $L_{\text{eq}} = \sum_{n=1}^N L_n$ .

$$\mathcal{E}_L = -L \frac{di}{dt} \quad (\text{self-induced emf}). \quad (30-35)$$

**48** *Inductors in parallel.* Two inductors  $L_1$  and  $L_2$  are connected in parallel and separated by a large distance so that the magnetic field of one cannot affect the other. (a) Show that the equivalent inductance is given by

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2}.$$

48. (a) Voltage is proportional to inductance (by Eq. 30-35) just as, for resistors, it is proportional to resistance. Now, the (independent) voltages for parallel elements are equal ( $V_1 = V_2$ ), and the currents (which are generally functions of time) add ( $i_1(t) + i_2(t) = i(t)$ ). This leads to the Eq. 27-21 for resistors. We note that this condition on the currents implies

$$\frac{di_1(t)}{dt} + \frac{di_2(t)}{dt} = \frac{di(t)}{dt}.$$

Thus, although the inductance equation Eq. 30-35 involves the rate of change of current, as opposed to current itself, the conditions that led to the parallel resistor formula also apply to inductors. Therefore,

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2}.$$

Note that to ensure the independence of the voltage values, it is important that the inductors not be too close together (the related topic of mutual inductance is treated in Section 30-12). The requirement is that the field of one inductor not to have significant influence (or “coupling”) in the next.

(b) Just as with resistors,  $\frac{1}{L_{\text{eq}}} = \sum_{n=1}^N \frac{1}{L_n}$ .