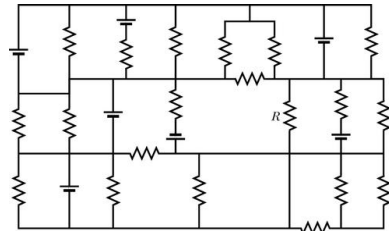


## Physics 2102

### Circuits



### DC circuits: resistances in series

Two resistors are “in series” if they are connected such that the **same current** flows in both.


The “equivalent resistance” is a single imaginary resistor that can replace the resistances in series.

“Walking the loop” results in :

$$E - iR_1 - iR_2 - iR_3 = 0 \rightarrow i = E / (R_1 + R_2 + R_3)$$

In the circuit with the equivalent resistance,
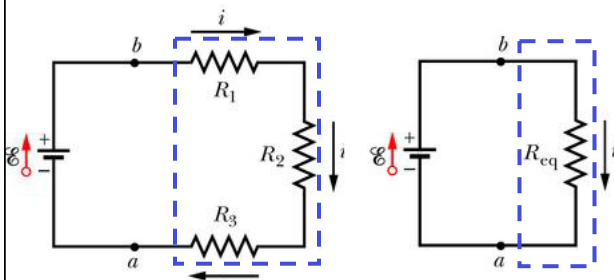
$$E - iR_{eq} = 0 \rightarrow i = E / R_{eq}$$



Thus,

$$R_{eq} = \sum_{j=1}^n R_j$$

## Multiloop circuits: resistors in parallel

Two resistors are “in parallel” if they are connected such that there is the **same potential** drop through both.

The “equivalent resistance” is a single imaginary resistor that can replace the resistances in parallel.



“Walking the loops” results in :

$$E - i_1 R_1 = 0, E - i_2 R_2 = 0, E - i_3 R_3 = 0$$

The total current delivered by the battery is  $i = i_1 + i_2 + i_3 = E/R_1 + E/R_2 + E/R_3$ .

In the circuit with the equivalent resistor,  $i = E/R_{eq}$ . Thus,
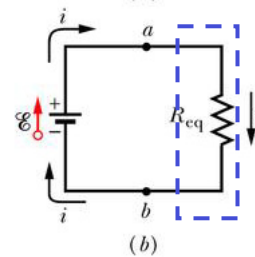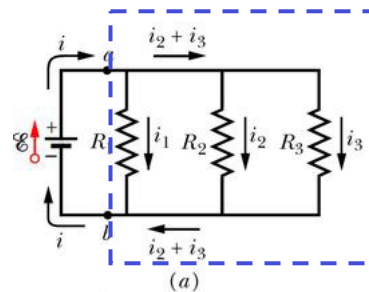
$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$



## Resistors and Capacitors


### Resistors



Key formula:  $V = iR$

In series: same current

$$R_{eq} = \sum R_j$$

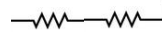

In parallel: same voltage

$$1/R_{eq} = \sum 1/R_j$$




### Capacitors



$Q = CV$


same charge

$$1/C_{eq} = \sum 1/C_j$$

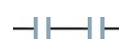


same voltage

$$C_{eq} = \sum C_j$$

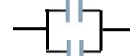

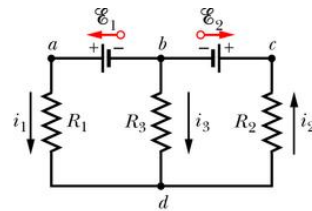
## DC circuits

- **Loop rule:** when walking along a loop, add potential differences across each element, and make the total equal to zero when you come back to the original point.
- **Junction rule:** at every junction, total current is conserved.
- Problem strategy:
  - Replace resistors in series and in parallel with their equivalent resistors
  - Draw currents in every wire, and label them
  - Write the loop rule for each loop (or for the loop that involves your question)
  - Write the junction rules for the currents.
  - Solve the equations for the currents.
  - Answer the question that was asked.


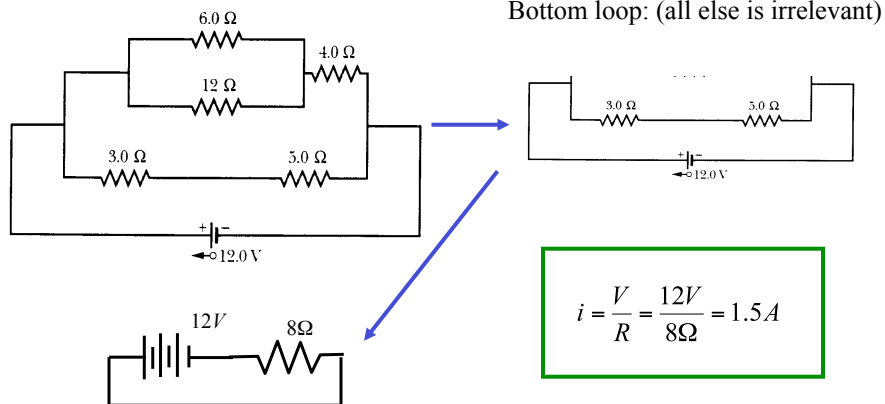
## Example


**38E.** A circuit containing five resistors connected to a battery with a 12.0 V emf is shown in Fig. 28-38. What is the potential difference across the 5.0 Ω resistor?



Which resistor gets hotter?

## Example

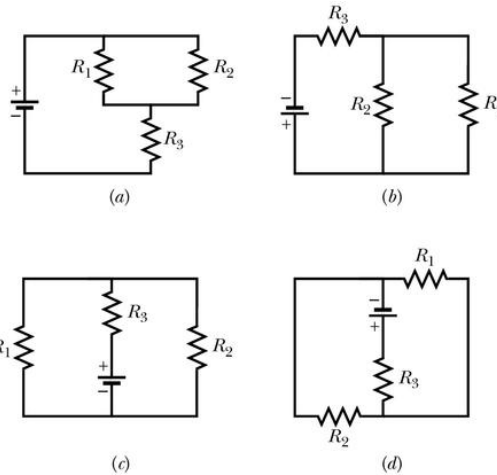
- a) Which circuit has the largest equivalent resistance?
- b) Assuming that all resistors are the same, which one dissipates more power?
- c) Which resistor has the smallest potential difference across it?


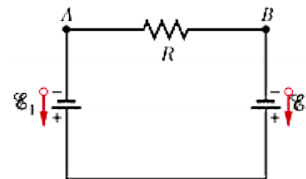
## Example

Assume the batteries are ideal, and have emf  $E_1=12\text{V}$ ,  $E_2=9\text{V}$ , and  $R=3\Omega$ .

- Which way will the current flow?
- Which battery is doing positive work?
- If the potential at A is 0V, what is the potential at B?
- How much power is dissipated by the resistor?
- How much power is dissipated (or absorbed) by the batteries?




## Example

Find the equivalent resistance between points

(a)  $F$  and  $H$  and

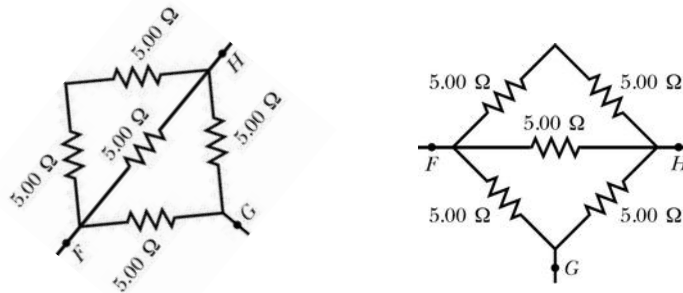
(b)  $F$  and  $G$ .

(Hint: For each pair of points, imagine that a battery is connected across the pair.)



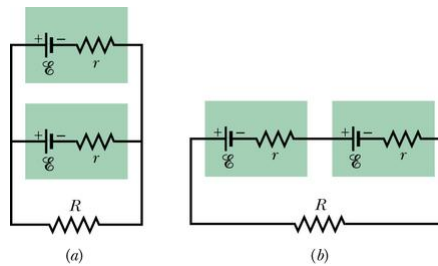
## Non-ideal batteries

- You have two ideal identical batteries, and a resistor. Do you connect the batteries in series or in parallel to get maximum current through  $R$ ?
- Does the answer change if you have non-ideal (but still identical) batteries?



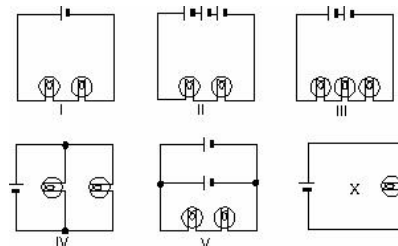
## Light bulbs

- If all batteries are ideal, and all batteries and lightbulbs are identical, in which arrangements will the lightbulbs as bright as the one in circuit X?
- Does the answer change if batteries are not ideal?


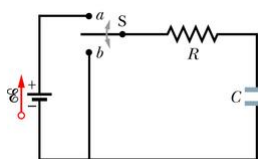
## RC circuits: charging a capacitor

In these circuits, current will change for a while, and then stay constant. We want to solve for current as a function of time  $i(t)$ . The charge on the capacitor will also be a function of time:  $q(t)$ . The voltage across the resistor and the capacitor also change with time. To charge the capacitor, close the switch on  $a$ .



$$E + V_R(t) + V_C(t) = 0$$



$$E - i(t)R - q(t)/C = 0$$

$$E - (dq(t)/dt) R - q(t)/C = 0$$


A differential equation for  $q(t)$ ! The solution is:

$$q(t) = CE(1 - e^{-t/RC})$$

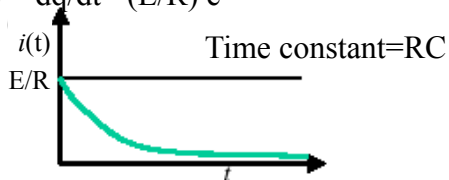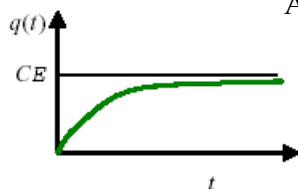And then  $i(t) = dq/dt = (E/R) e^{-t/RC}$



## RC circuits: discharging a capacitor

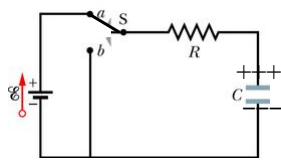

Assume the switch has been closed on *a* for a long time: the capacitor will be charged with  $Q=CE$ .




Then, close the switch on *b*: charges find their way across the circuit, establishing a current.

$$V_R + V_C = 0$$

$$-i(t)R + q(t)/C = 0 \Rightarrow (dq/dt)R + q(t)/C = 0$$

$$\text{Solution: } q(t) = q_0 e^{-t/RC} = CE e^{-t/RC}$$

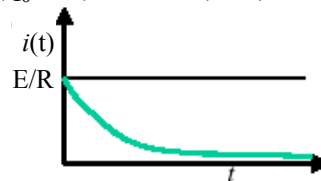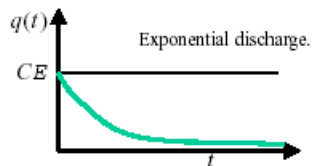
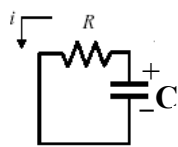
$$i(t) = dq/dt = (q_0/RC) e^{-t/RC} = (E/R) e^{-t/RC}$$


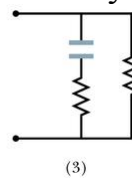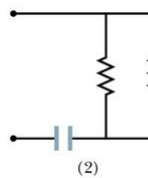
## Example

The three circuits below are connected to the same ideal battery with emf  $E$ . All resistors have resistance  $R$ , and all capacitors have capacitance  $C$ .

- Which capacitor takes the longest in getting charged?
- Which capacitor ends up with the largest charge?
- What's the final current delivered by each battery?
- What happens when we disconnect the battery?



## Example

In the figure,  $E = 1 \text{ kV}$ ,  $C = 10 \text{ } \mu\text{F}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ . With  $C$  completely uncharged, switch  $S$  is suddenly closed (at  $t = 0$ ).

- What's the current through each resistor at  $t=0$ ?
- What's the current through each resistor after a long time?
- How long is a long time?

