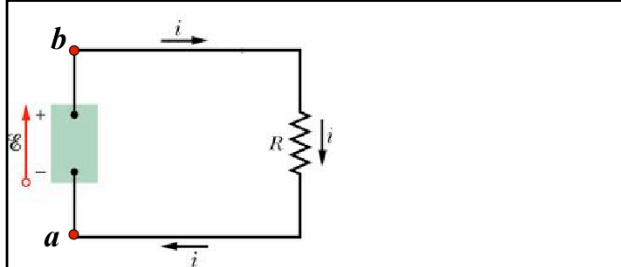





Physics 2102  
Gabriela González



# Physics 2102

## Circuits

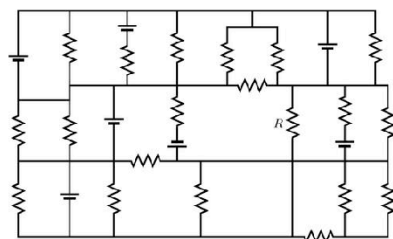

## Recall: Resistors and Capacitors


### Resistors



Key formula:  $V=iR$


In series: same current

$$R_{eq} = \sum R_j$$

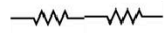

In parallel: same voltage

$$1/R_{eq} = \sum 1/R_j$$

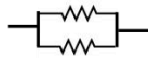


### Capacitors



$Q=CV$


same charge

$$1/C_{eq} = \sum 1/C_j$$

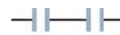


same voltage

$$C_{eq} = \sum C_j$$

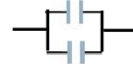

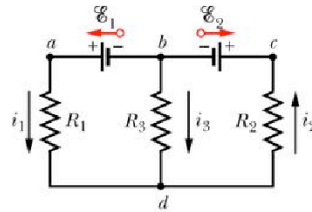
## Recall: DC circuits

- **Loop rule:** when walking along a loop, add potential differences across each element, and make the total equal to zero when you come back to the original point.
- **Junction rule:** at every junction, total current is conserved.
- Problem strategy:
  - Replace resistors in series and in parallel with their equivalent resistors
  - Draw currents in every wire, and label them
  - Write the loop rule for each loop (or for the loop that involves your question)
  - Write the junction rules for the currents.
  - Solve the equations for the currents.
  - Answer the question that was asked.



## Example

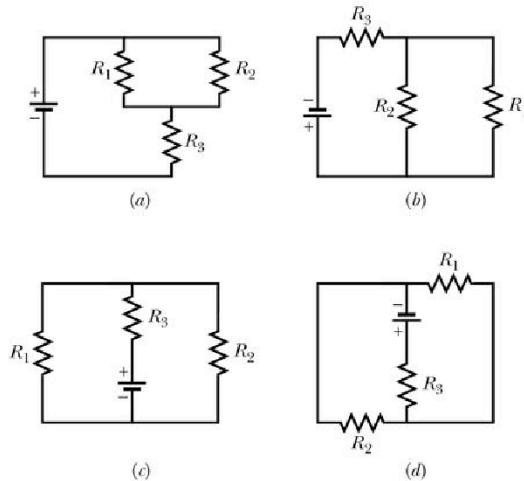- a) Which circuit has the largest equivalent resistance?
- b) Assuming that all resistors are the same, which one dissipates more power?
- c) Which resistor has the smallest potential difference across it?



(a) All circuits have the same equivalent resistance: In all cases,  $R_1$  and  $R_2$  are in parallel, and the equivalent resistor  $R_{12} = 1 / (1/R_1 + 1/R_2) = R_1 R_2 / (R_1 + R_2)$  is in series with  $R_3$ , so

$$R_{123} = R_3 + R_1 R_2 / (R_1 + R_2)$$


(b) If all resistors are the same, we use  $P = i^2 R$ , so the one with largest current will dissipate more power: that is  $R_3$ . The current through  $R_1$  and  $R_2$  is only half, so each of them will dissipate  $1/4$  the power dissipated by  $R_3$ .

(c) If the current through the battery and  $R_3$  is  $I$ , the voltage across  $R_3$  is  $V_3 = IR$ . Since only half the current goes through each of  $R_1$  and  $R_2$ , then  $V_1 = V_2 = IR/2$ . Thus,  $R_1$  and  $R_2$  have the smallest potential difference across them.
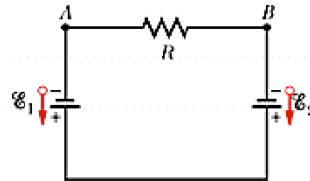
## Example

Assume the batteries are ideal, and have emf  $E_1=12\text{V}$ ,  $E_2=9\text{V}$ , and  $R=3\Omega$ .

- Which way will the current flow?
- Which battery is doing positive work?
- If the potential at A is  $0\text{V}$ , what is the potential at B?
- How much power is dissipated by the resistor?
- How much power is delivered (or absorbed) by the batteries?



- The current will flow from A to B through the batteries (counterclockwise).
- $E_1$  is doing positive work,  $E_2$  is doing negative work (as in a car battery getting charged)
- Voltage difference between A and B is the voltage difference of the batteries,  $+3\text{V}$  (B is at a higher potential).
- Current is  $3\text{Volts}/3\text{Ohms}=1\text{Amp}$ , so power dissipated by resistor is  $P=i^2 R = 3\text{ Watts}$ .
- $E_1$  delivers  $P=iV=12\text{ Watts}$ , while  $E_2$  absorbs  $P=iV= 9\text{ Watts}$ .


## Example

Find the equivalent resistance between points

(a)  $F$  and  $H$  and

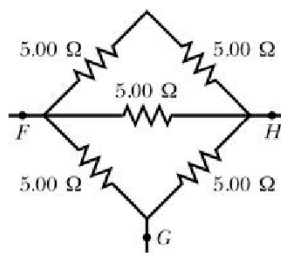(b)  $F$  and  $G$ .

(Hint: For each pair of points, imagine that a battery is connected across the pair.)




(a) There are three paths for current, or three resistors in parallel;; top and bottom paths have two resistors in series. The three parallel paths have: 10 Ohms on top path, 5 Ohms in middle path, 10 Ohms in bottom path; equivalent resistance is then  $1/(1/10+1/5+1/10)=1/(4/10)=10/4=2.5$  Ohms.

(b) We first replace top resistors in series with the 10 Ohms equivalent; this 10 Ohms is in parallel with 5 Ohms, resulting in  $3/10$  Ohms. That one is now in series with 5 Ohms between  $H$  and  $G$ , resulting in 5.3 Ohms, now in parallel with 5 Ohms between  $F$  and  $G$ . The total equivalent resistance is then  $1/(1/5.3+1/5)=2.6$  Ohms.
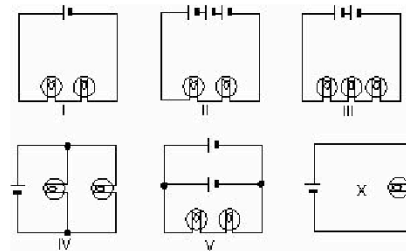
## Light bulbs

- If all batteries are ideal, and all batteries and lightbulbs are identical, in which arrangements will the lightbulbs as bright as the one in circuit X?



Power through a light bulb is  $P=i^2R$ . In X, with  $i=V/R$ .

In (i),  $i=E/2R$ : dimmer.

In (ii),  $i=2E/2R=E/R$ : same as in X.

In (iii),  $i=2E/3R$ : dimmer.

In (iv), current through the battery is  $i=E/(R/2)=2E/R$ , but current through each light bulb is  $E/R$ ; same as in X.

In (v),  $i=E/(2R)$ : dimmer.

So, (ii) and (iv) are as bright as X.

## RC circuits: charging a capacitor


In these circuits, current will change for a while, and then stay constant.

We want to solve for current as a function of time  $i(t)$ .

The charge on the capacitor will also be a function of time:  $q(t)$ .

The voltage across the resistor and the capacitor also change with time.

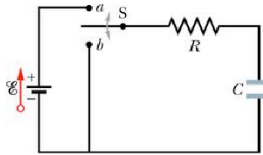To charge the capacitor, close the switch on  $a$ .



$$E + V_R(t) + V_C(t) = 0$$



$$E - i(t)R - q(t)/C = 0$$

$$E - (dq(t)/dt)R - q(t)/C = 0$$

A differential equation for  $q(t)$ ! The solution is:


$$q(t) = CE(1 - e^{-t/RC})$$

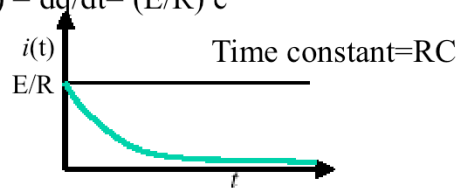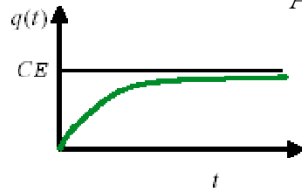And then  $i(t) = dq/dt = (E/R) e^{-t/RC}$





## RC circuits: discharging a capacitor

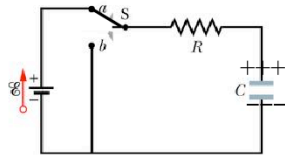

Assume the switch has been closed on *a* for a long time: the capacitor will be charged with  $Q=CE$ .




Then, close the switch on *b*: charges find their way across the circuit, establishing a current.

$$V_R + V_C = 0$$

$$-i(t)R + q(t)/C = 0 \Rightarrow (dq/dt)R + q(t)/C = 0$$

$$\text{Solution: } q(t) = q_0 e^{-t/RC} = CE e^{-t/RC}$$

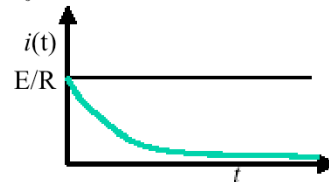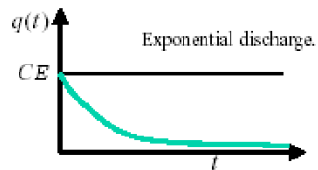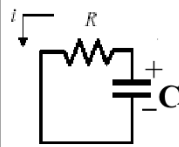
$$i(t) = dq/dt = (q_0/RC) e^{-t/RC} = (E/R) e^{-t/RC}$$


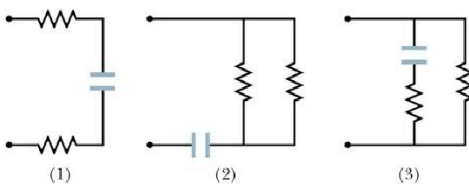
## Example

The three circuits below are connected to the same ideal battery with emf  $E$ . All resistors have resistance  $R$ , and all capacitors have capacitance  $C$ .

- Which capacitor takes the longest in getting charged?
- Which capacitor ends up with the largest charge?
- What's the final current delivered by each battery?
- What happens when we disconnect the battery?




- Time constants are  $2RC$ ,  $RC/2$ ,  $RC$ , so Capacitor in (1) takes the longest.
- $Q=CV$ , and in all cases,  $V=E$  at the final equilibrium.
- Batteries in (1) and (2) do not deliver any current when the capacitor is charged; Battery in (3) will deliver a current  $i=E/R$ .
- Capacitor will stay charged in (1) and (2); charge in capacitor (3) will start a current, and will get discharged with a time constant  $2RC$ .
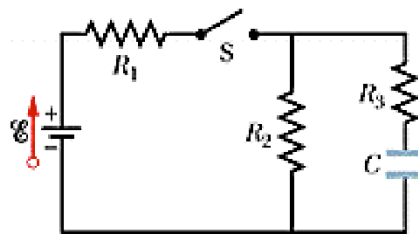
## Example

In the figure,  $E = 1 \text{ kV}$ ,  $C = 10 \text{ } \mu\text{F}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ . With  $C$  completely uncharged, switch  $S$  is suddenly closed (at  $t = 0$ ).

- What's the current through each resistor at  $t=0$ ?
- What's the current through each resistor after a long time?
- How long is a long time?



- At  $t=0$ , there is no voltage across the capacitor, so  $R_2$  and  $R_3$  are in parallel, with a total equivalent resistance equal to  $1.5 \text{ M}\Omega$ , and the battery delivers a total current  $i = 1\text{kV}/1.5\text{M}\Omega = 0.67 \text{ mA}$ .: we have  $0.67 \text{ mA}$  through  $R_1$ , and half that ( $0.33 \text{ mA}$ ) through each of  $R_2$  and  $R_3$ .
- After a long time, the capacitor is charged, no current flows through  $R_3$ , and  $R_2$  and  $R_3$  are in series, with a total equivalent resistance equal to  $2 \text{ M}\Omega$ , and a battery delivered by the battery of  $1\text{kV}/2\text{M}\Omega = 0.5 \text{ mA}$ : this current flows through  $R_1$  and  $R_2$ .
- The time constant for the capacitor getting charged is  $1\text{M}\Omega \times 10 \text{ } \mu\text{F} = 10 \text{ sec}$  : we need to wait tens of seconds.