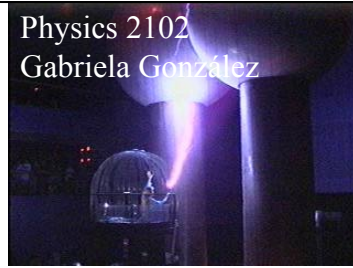


Physics 2102  
Gabriela González




## Physics 2102

### Capacitors


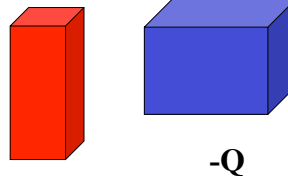
## Capacitors and Capacitance

Capacitor: any two conductors,  
one with charge  $+Q$ , other  
with charge  $-Q$



Potential DIFFERENCE between  
conductors =  $V$

$$Q = CV \text{ -- } C = \text{capacitance}$$

Units of capacitance:

**Farad** (F) = Coulomb/Volt

Uses: storing and releasing  
electric charge/energy.

Most electronic capacitors:  
micro-Farads ( $\mu\text{F}$ ),


pico-Farads (pF) --  $10^{-12}$  F

New technology:


compact 1 F capacitors
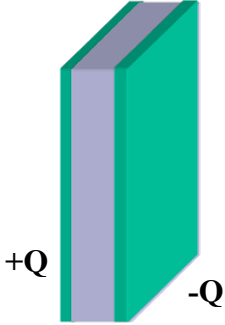
# Capacitance

- Capacitance depends only on GEOMETRICAL factors and on the MATERIAL that separates the two conductors
- e.g. Area of conductors, separation, whether the space in between is filled with air, plastic, etc.




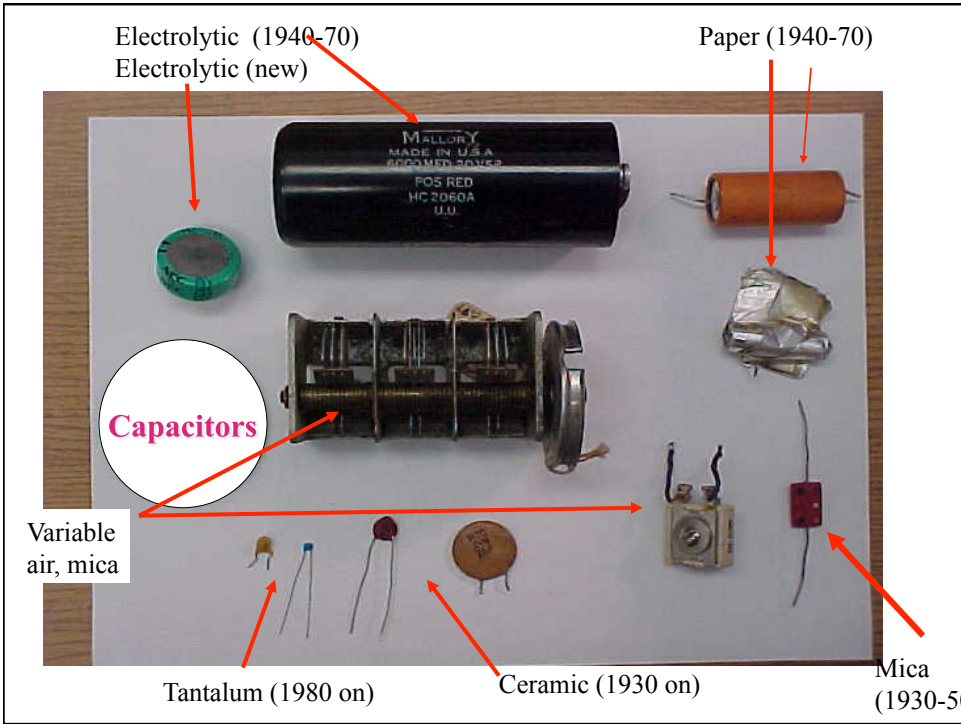(We first focus on capacitors where gap is filled by AIR!)


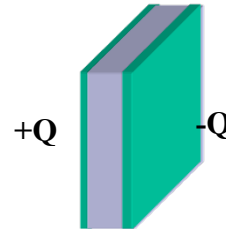
## Capacitors and Capacitance

Capacitor: any two conductors,  
one with charge  $+Q$ , other  
with charge  $-Q$



Potential DIFFERENCE between  
conductors =  $V$

$$Q = CV \quad C = \text{capacitance}$$

Units of capacitance:

**Farad** (F) = Coulomb/Volt

Uses: storing and releasing  
electric charge/energy.

Most electronic capacitors:  
micro-Farads ( $\mu\text{F}$ ),  
pico-Farads (pF) --  $10^{-12}$  F

New technology:  
compact 1 F capacitors

## Parallel Plate Capacitor

We want *capacitance*:  $C=Q/V$

E field between the plates: (Gauss' Law)

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$


Area of each plate =  $A$   
Separation =  $d$   
charge/area =  $\sigma = Q/A$

Relate E to potential difference V:

$$V = \int_0^d \vec{E} \cdot d\vec{x} = \int_0^d \frac{Q}{\epsilon_0 A} dx = \frac{Qd}{\epsilon_0 A}$$

What is the capacitance C?
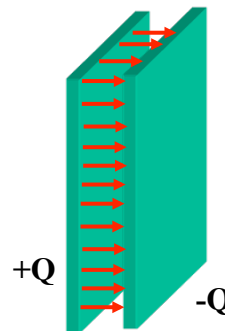
$$C = \frac{Q}{V} = \frac{\epsilon_0 A}{d}$$



## Parallel Plate Capacitor -- example

- A huge parallel plate capacitor consists of two square metal plates of side 50 cm, separated by an air gap of 1 mm
- What is the capacitance?
- $C = \epsilon_0 A/d =$   
 $(8.85 \times 10^{-12} \text{ F/m})(0.25 \text{ m}^2)/(0.001 \text{ m})$   
 $= 2.21 \times 10^{-9} \text{ F}$   
(small!!)


**Lesson: difficult to get large values of capacitance without special tricks!**

## Isolated Parallel Plate Capacitor

$$C = \frac{Q}{V} = \frac{Q}{Ed} = \frac{\epsilon_0 A}{d}$$

- A parallel plate capacitor of capacitance  $C$  is charged using a battery.
  - Charge =  $Q$ , potential difference =  $V$ .
  - Battery is then disconnected.
  - If the plate separation is INCREASED, does potential difference  $V$ :
- (a) Increase?  
(b) Remain the same?  
(c) Decrease?

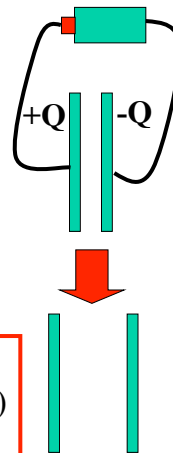- $Q$  is fixed!
- $C$  decreases ( $=\epsilon_0 A/d$ )
- $Q=CV$ ;  $V$  increases.



## Parallel Plate Capacitor & Battery


$$C = \frac{Q}{V} = \frac{Q}{Ed} = \frac{\epsilon_0 A}{d}$$

- A parallel plate capacitor of capacitance  $C$  is charged using a battery.
- Charge =  $Q$ , potential difference =  $V$ .
- Plate separation is INCREASED while battery remains connected.

Does the electric field inside:

- Increase?
- Remain the same?
- Decrease?

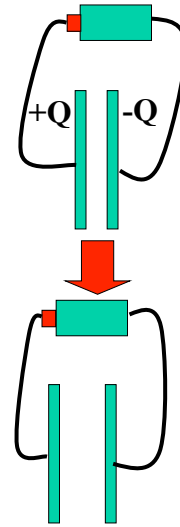
- $V$  is fixed by battery!
- $C$  decreases ( $=\epsilon_0 A/d$ )
- $Q=CV$ ;  $Q$  decreases
- $E = Q/\epsilon_0 A$  decreases



## Spherical Capacitor

What is the electric field inside the capacitor? (Gauss' Law)

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

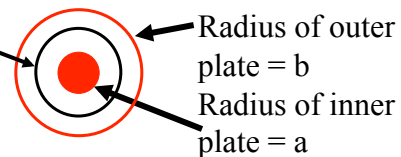

Concentric spherical shells:  
Charge  $+Q$  on inner shell,  
 $-Q$  on outer shell

Relate  $E$  to potential difference between the plates:

$$V = \int_a^b \vec{E} \cdot d\vec{r} = \int_a^b \frac{kQ}{r^2} dr = \left[ -\frac{kQ}{r} \right]_a^b = kQ \left[ \frac{1}{a} - \frac{1}{b} \right]$$


## Spherical Capacitor

What is the capacitance?

$$C = Q/V =$$

$$= \frac{Q}{4\pi\epsilon_0 \left[ \frac{1}{a} - \frac{1}{b} \right]}$$

$$= \frac{4\pi\epsilon_0 ab}{(b-a)}$$

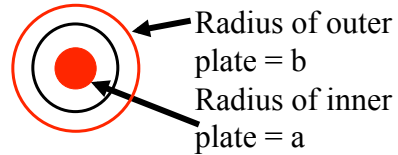

Concentric spherical shells:  
Charge +Q on inner shell,  
-Q on outer shell

Isolated sphere: let  $b \gg a$ ,

$$C = 4\pi\epsilon_0 a$$

## Cylindrical Capacitor


What is the electric field in between the plates?

$$E = \frac{Q}{2\pi\epsilon_0 rL}$$


Relate E to potential difference between the plates:

$$V = \int_a^b \vec{E} \cdot d\vec{r}$$
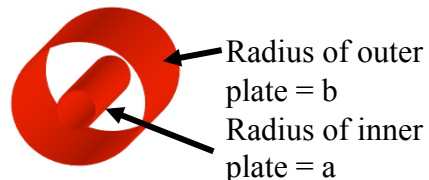
$$= \int_a^b \frac{Q}{2\pi\epsilon_0 rL} dr = \left[ \frac{Q \ln r}{2\pi\epsilon_0 L} \right]_a^b = \frac{Q}{2\pi\epsilon_0 L} \ln\left(\frac{b}{a}\right)$$



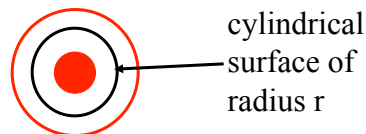Length of capacitor = L  
+Q on inner rod, -Q on outer shell




## Cylindrical Capacitor

What is the capacitance C?

$$C = Q/V = \frac{Q}{\frac{Q}{2\pi\epsilon_0 L \ln\left(\frac{b}{a}\right)}}$$
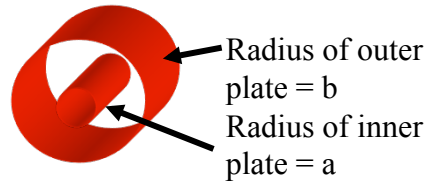
$$= \frac{2\pi\epsilon_0 L}{\ln\left(\frac{b}{a}\right)}$$



Length of capacitor = L  
Charge +Q on inner rod,  
-Q on outer shell

Example: co-axial cable.


## Summary

- Any two charged conductors form a capacitor.
- Capacitance :  $C = Q/V$
- Simple Capacitors:

*Parallel plates:*  $C = \epsilon_0 A/d$


*Spherical :*  $C = 4\pi \epsilon_0 ab/(b-a)$

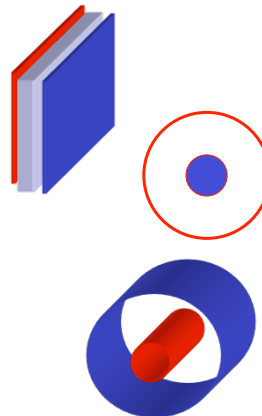*Cylindrical:*  $C = 2\pi \epsilon_0 L/\ln(b/a)$


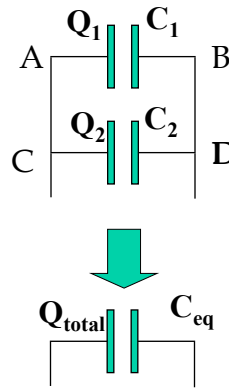
## Capacitors in Parallel

- A wire is a conductor, so it is an equipotential.
- Capacitors in parallel have SAME potential difference but NOT ALWAYS same charge.
- $V_{AB} = V_{CD} = V$
- $Q_{\text{total}} = Q_1 + Q_2$
- $C_{\text{eq}}V = C_1V + C_2V$
- $C_{\text{eq}} = C_1 + C_2$
- **Equivalent parallel capacitance = sum of capacitances**



### PARALLEL:


- V is same for all capacitors
- Total charge in  $C_{\text{eq}}$  = sum of charges

## Capacitors in series

- $Q_1 = Q_2 = Q$  (WHY??)
- $V_{AC} = V_{AB} + V_{BC}$

$$\frac{Q}{C_{\text{eq}}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$
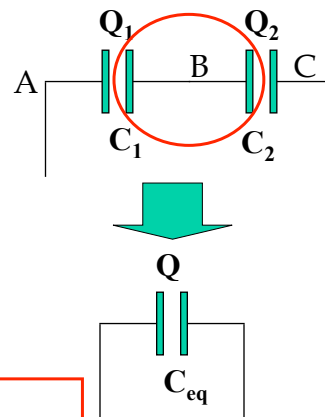
$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$



### SERIES:


- Q is same for all capacitors
- Total potential difference in  $C_{\text{eq}}$  = sum of V


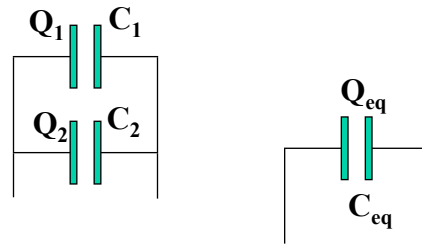
## Capacitors in parallel and in series


- **In parallel :**

- $C_{eq} = C_1 + C_2$
- $V_{eq} = V_1 = V_2$
- $Q_{eq} = Q_1 + Q_2$



- **In series :**

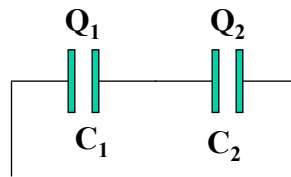- $1/C_{eq} = 1/C_1 + 1/C_2$
- $V_{eq} = V_1 + V_2$
- $Q_{eq} = Q_1 = Q_2$




## Example 1

**What is the charge on each capacitor?**

- $Q = CV$ ;  $V = 120 \text{ V}$
- $Q_1 = (10 \mu\text{F})(120\text{V}) = 1200 \mu\text{C}$
- $Q_2 = (20 \mu\text{F})(120\text{V}) = 2400 \mu\text{C}$
- $Q_3 = (30 \mu\text{F})(120\text{V}) = 3600 \mu\text{C}$

Note that:

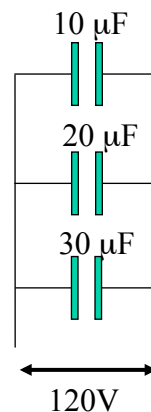- Total charge ( $7200 \mu\text{C}$ ) is shared between the 3 capacitors in the ratio  $C_1:C_2:C_3$  -- i.e. 1:2:3




## Example 2

What is the potential difference across each capacitor?

- $Q = CV$ ;  $Q$  is same for all capacitors
- Combined  $C$  is given by:
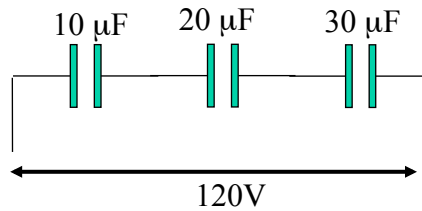
$$\frac{1}{C_{eq}} = \frac{1}{(10\mu F)} + \frac{1}{(20\mu F)} + \frac{1}{(30\mu F)}$$




- $C_{eq} = 5.46 \mu F$
- $Q = CV = (5.46 \mu F)(120V) = 655 \mu C$
- $V_1 = Q/C_1 = (655 \mu C)/(10 \mu F) = 65.5 V$
- $V_2 = Q/C_2 = (655 \mu C)/(20 \mu F) = 32.75 V$
- $V_3 = Q/C_3 = (655 \mu C)/(30 \mu F) = 21.8 V$

Note: 120V is shared in the ratio of INVERSE capacitances i.e. 1:(1/2):(1/3)  
(largest  $C$  gets smallest  $V$ )
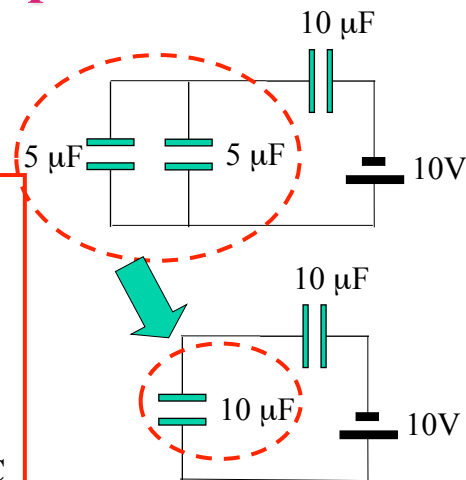
## Example 3


In the circuit shown, what is the charge on the  $10\mu F$  capacitor?

- The two  $5\mu F$  capacitors are in parallel
- Replace by  $10\mu F$
- Then, we have two  $10\mu F$  capacitors in series
- So, there is 5V across the  $10\mu F$  capacitor of interest
- Hence,  $Q = (10\mu F)(5V) = 50\mu C$


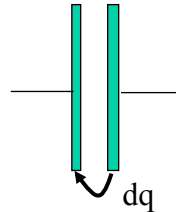
## Energy Stored in a Capacitor

- Start out with uncharged capacitor
- Transfer small amount of charge  $dq$  from one plate to the other until charge on each plate has magnitude  $Q$
- How much work was needed?



$$U = \int_0^Q V dq = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C} = \frac{CV^2}{2}$$

## Energy Stored in Electric Field

- Energy stored in capacitor:  $U = Q^2/(2C) = CV^2/2$
- View the energy as stored in ELECTRIC FIELD
- For example, parallel plate capacitor:

**Energy DENSITY** = energy/volume =  $u =$


$$U = \frac{Q^2}{2CAd} = \frac{Q^2}{2\left(\frac{\epsilon_0 A}{d}\right)Ad} = \frac{Q^2}{2\epsilon_0 A^2} = \frac{\epsilon_0}{2} \left(\frac{Q}{\epsilon_0 A}\right)^2 = \frac{\epsilon_0 E^2}{2}$$

$\uparrow$   
 volume =  $Ad$

General expression for any region with vacuum (or air)
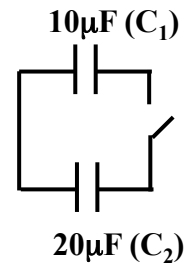
## Example

- **10 $\mu$ F capacitor is initially charged to 120V.**  
**20 $\mu$ F capacitor is initially uncharged.**
- **Switch is closed, equilibrium is reached.**
- **How much energy is dissipated in the process?**



Initial charge on 10 $\mu$ F = (10 $\mu$ F)(120V) = 1200 $\mu$ C

After switch is closed, let charges =  $Q_1$  and  $Q_2$ .

Charge is conserved:  $Q_1 + Q_2 = 1200\mu\text{C}$

Also,  $V_{\text{final}}$  is same:  $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow Q_1 = \frac{Q_2}{2}$

- $Q_1 = 400\mu\text{C}$
- $Q_2 = 800\mu\text{C}$
- $V_{\text{final}} = Q_1/C_1 = 40\text{ V}$


Initial energy stored =  $(1/2)C_1 V_{\text{initial}}^2 = (0.5)(10\mu\text{F})(120)^2 = 72\text{mJ}$

Final energy stored =  $(1/2)(C_1 + C_2)V_{\text{final}}^2 = (0.5)(30\mu\text{F})(40)^2 = 24\text{mJ}$

Energy lost (dissipated) = 48mJ

## Dielectric Constant

**DIELECTRIC**

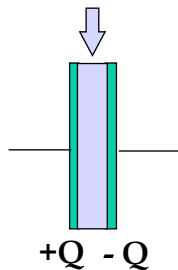


$$C = \kappa \epsilon_0 A/d$$

- If the space between capacitor plates is filled by a dielectric, the capacitance **INCREASES** by a factor  $\kappa$
- This is a useful, working definition for dielectric constant.
- Typical values of  $\kappa$ : 10 - 200

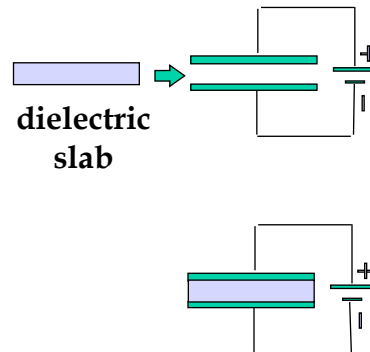
## Example

- Capacitor has charge  $Q$ , voltage  $V$
- Battery remains connected while dielectric slab is inserted.
- Do the following increase, decrease or stay the same:
  - Potential difference?
  - Capacitance?
  - Charge?
  - Electric field?


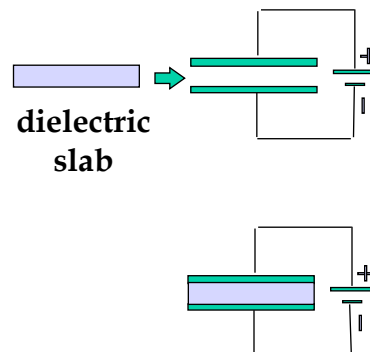
## Example (soln)

- Initial values:  
capacitance =  $C$ ; charge =  $Q$ ;  
potential difference =  $V$ ;  
electric field =  $E$ ;
- Battery remains connected
- $V$  is FIXED;  $V_{\text{new}} = V$  (**same**)
- $C_{\text{new}} = \kappa C$  (**increases**)
- $Q_{\text{new}} = (\kappa C)V = \kappa Q$  (**increases**).
- Since  $V_{\text{new}} = V$ ,  $E_{\text{new}} = E$  (**same**)



Energy stored?  $u = \epsilon_0 E^2 / 2 \Rightarrow u = \kappa \epsilon_0 E^2 / 2 = \epsilon E^2 / 2$

## Summary

- Capacitors in series and in parallel:
  - in series: charge is the same, potential adds, equivalent capacitance is given by  $1/C=1/C_1+1/C_2$
  - in parallel: charge adds, potential is the same, equivalent capacitance is given by  $C=C_1+C_2$ .
- Energy in a capacitor:  $U=Q^2/2C=CV^2/2$ ; energy density  $u=\epsilon_0 E^2/2$
- Capacitor with a dielectric: capacitance increases  $C'=\kappa C$